



Faculty of Engineering & Technology

Electrical & Computer Engineering Department

ADVANCED DIGITAL SYSTEMS DESIGN

ENCS3310

PROJECT

Introduction and background

This project is a digital circuit design for traffic light system for two roads and its test bench. The figure below shows the traffic and the table below shows the states of the traffic lights and the time they take.

 


Figure 1

State	Highway TL1	Highway TL2	Farm TL1	Farm TL2	Delay [Sec]
S0	Red	Red	Red	Red	1
S1	Red-Yellow	Red-Yellow	Red	Red	2
S2	Green	Green	Red	Red	30
S3	Green	Yellow	Red	Red	2
S4	Green	Red	Red	Red	10
S5	Yellow	Red	Red	Red	2
S6	Red	Red	Red	Red	1
S7	Red	Red	Red-Yellow	Red-Yellow	2
S8	Red	Red	Green	Green	15
S9	Red	Red	Green	Yellow	2
S10	Red	Red	Green	Red	5
S11	Red	Red	Yellow	Red-Yellow	2
S12	Red	Red	Red	Green	10
S13	Red	Red	Red	Yellow	2
S14	Red	Red	Red	Red	1
S15	Red	Red-Yellow	Red	Red	2
S16	Red	Green	Red	Red	15
S17	Red	Yellow	Red	Red	3

Table 1

Design philosophy

The main module **traffic_light** is consists of controller and counter where counter used to know the time (number of the clock where a clock takes 1s) and controller turn on traffic lights on the proper time for the proper duration.

The main module **traffic_light** code:

```
module traffic_light(input clk, go, rst, output [1:0] highwaySignal1, highwaySignal2,
farmSignal1, farmSignal2);
    wire [6:0] count;
    counter CTR(go, rst, clk, count);
    controller CRL(clk, rst, count, highwaySignal1, highwaySignal2, farmSignal1,
farmSignal2);
endmodule
```

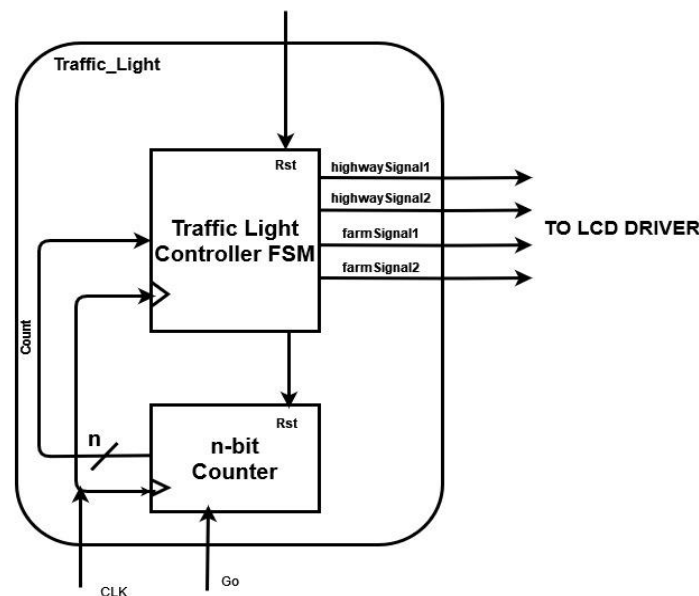


Figure 2 - traffic_light

Counter module when positive edge appears the output count increment by one until 107 it will reset to zero. But if 'go' input is low '0' then the count will stop incrementing and freezes. Also when reset input 'rst' is high '1' then the count will clear and become zero.

Counter module code:

```
module counter(input go, rst, clk, output reg [6:0] count=0);
    always@(posedge clk) begin
        if(rst) count = 0;
        else if(go)
            if(count>=107) count=0;
            else count++;
    end
endmodule
```

Controller module move to the next state by use an array included the time when a specific state become ('{1,3,33,35,45,47,48,50,65,67,72,74,84,86,87,89,104,107}' this array is the same as accumulated delay). The table below shows when farms traffic lights change with orange color and when highway traffic lights change with blue color. Moreover the darker color shows the specific street light that changes on any state. Also from the table can be figure that the way the lights change is by increment there light code. So in this design as you can see in the code below, when the positive edge of the clock becomes and according to states array if new state time is become, then it cheek if this is the state that the traffic light changes on if yes increment the code of the colors of the traffic light otherwise do not anything.

00 : Green

01 : Yellow (when changing from green)

10 : Red

11 : Red-Yellow (when changing from red)

State	Highway TL1	Highway TL2	Farm TL1	Farm TL2	Delay [Sec]	state when clk
S0	10	10	10	10	1	0 and 107
S1	11	11	10	10	2	1
S2	00	00	10	10	30	3
S3	00	01	10	10	2	33
S4	00	10	10	10	10	35
S5	01	10	10	10	2	45
S6	10	10	10	10	1	47
S7	10	10	11	11	2	48
S8	10	10	00	00	15	50
S9	10	10	00	01	2	65
S10	10	10	00	10	5	67
S11	10	10	01	11	2	72
S12	10	10	10	00	10	74
S13	10	10	10	01	2	84
S14	10	10	10	10	1	86
S15	10	11	10	10	2	87
S16	10	00	10	10	15	89
S17	10	01	10	10	3	104

Table 2

Controller module code:

```

module controller(input clk, rst, [6:0] count, output reg [1:0] highwaySignal1=2,
highwaySignal2=2, farmSignal1=2, farmSignal2=2);
    reg [6:0] state [0:17] =
    '{1,3,33,35,45,47,48,50,65,67,72,74,84,86,87,89,104,107}; //ppears in any clk
    reg [4:0] s = 0;
    always@(posedge clk && count >= state[s] && rst == 0) begin
        if(s >= 6 && s < 14) begin
            if((s <= 7) || (s >= 10 && s <= 11)) farmSignal1++;
            farmSignal2++;
        end
        else begin

```

```

        if((s >= 0 && s <= 1) || (s >= 4 && s <= 5)) highwaySignal1++;
        if((s >= 0 && s <= 3) || (s >= 14)) highwaySignal2++;
    end
    if(s == 17) s=0;
    else s++;
end
endmodule

```

traffic_light_TB module includes generate_test and analyzer. This module create 108 clocks where 107 is the last value that the counter reach it and use repeat(216) where clock has to change two times to get one positive edge ($108 \times 2 = 216$). Then this module test 'rst' input is high '1' and when 'go' input is low '0'. If the generator output values match the traffic light system output values then traffic_light_TB print "fault free". But if any values of results and expected results do not matched traffic_light_TB will receives high signal '1' from the analyzer at error wire then traffic_light_TB will stop clocking and error message will printed by the analyzer where that needs lees code.

traffic_light_TB code:

```

module traffic_light_TB();
    reg clk=0;
    reg go=1, rst=0;
    reg [7:0] expectedResult; reg [1:0] highwaySignal1; reg [1:0] highwaySignal2;
    reg [1:0] farmSignal1; reg [1:0] farmSignal2; reg [6:0] count;
    wire error;
    generate_test GT(clk, go, rst, count, expectedResult);
    traffic_light TL(clk, go, rst, highwaySignal1, highwaySignal2, farmSignal1,
farmSignal2);
    analyzer AZ(clk, count, {highwaySignal1, highwaySignal2, farmSignal1,
farmSignal2}, expectedResult, error);
    initial begin
        repeat(216) begin //(107clk + 1)*2
            #500ms if(error) break; //500ms*2 = 1s
            clk = ~clk;
        end
        if(!error) begin
            rst=1; #500ms clk = ~clk; #500ms clk = ~clk; //test reset
            rst=0; #500ms clk = ~clk; #500ms clk = ~clk;
        end
        if(!error) begin
            go=0; #500ms clk = ~clk; #500ms clk = ~clk; //test go
            go=1; #500ms clk = ~clk; #500ms clk = ~clk;
        end
        if(!error) $monitor("fault free");
    end
endmodule

```

generate_test module use memory method to generate the expected results where when the counter pass the indicated time of the previous state then change state number 's' and this state number is the same as the index number of the output values that stores in the memory that named 'state' where stores as 8bit blocks.

generate_test code:

```
module generate_test(input reg clk, reg go, reg rst, output reg [6:0] count=0, reg
[7:0] expectedResult);
    reg [6:0] state [0:17] =
'1,3,33,35,45,47,48,50,65,67,72,74,84,86,87,89,104,107};
    reg [4:0] s = 0;
    reg [7:0] results [0:17] = '{8'b10101010,8'b11111010,8'b00001010,8'b00011010,
8'b00101010,8'b01101010,8'b10101010,8'b10101111,8'b10100000,8'b10100001,
8'b10100010,8'b10100111,8'b10101000,8'b10101001,8'b10101010,8'b10111010,
8'b10001010,8'b10011010};
    initial expectedResult = results[s];
    always@(posedge clk) begin
        if(rst) count=0;
        else if(go) begin
            count++;
            if(count >= state[s])
                if(s == 17) begin
                    s=0;
                    count=0;
                end
            else s++;
            expectedResult = results[s];
        end
    end
endmodule
```

analyzer module sets the error flag to high 'one' and display error message with counter value when the error happens if a result value and corresponding expected value dose not matched.

analyzer module code:

```
module analyzer(input clk, [6:0] count, reg [7:0] result, reg [7:0] expectedResult,
output reg error = 0);
    always@(posedge clk or count == 0) begin
        #100ms;
        if(result != expectedResult) begin
            error = 1;
            $monitor("faulty when counter =%d\nresult = %b <and>
expectedResult = %b", count, result, expectedResult);
        end
    end
endmodule
```

Results

In the figures below (figure3 to 6) we can see that the test tell us that our system structure works as we want, and when added a deliberate error the test bench recognize it and tell when the error occur.

Normal condition:

```

59 module generate_test(input reg clk, reg go, reg rst, output reg [6:0] count=0, reg [7:0] expectedResult);
60 reg [6:0] state [0:17] = '{1,3,33,35,45,47,48,50,65,67,72,74,84,86,87,89,104,107};
61 reg [4:0] s = 0;
62 reg [7:0] results [0:17] = '{8'b10101010,8'b11111010,8'b00001010,8'b00011010,
63 8'b00101010,8'b01101010,8'b10101010,8'b10101111,8'b10100000,8'b10100001,
64 8'b10100010,8'b10100111,8'b10101000,8'b10101001,8'b10101010,8'b10111010,
65 8'b10001010,8'b10011010};
66 initial expectedResult = results[s];
67 always@(posedge clk) begin
68   if(rst) count=0;
69   else if(go) begin
70     count++;
71     if(count >= state[s])
72       if(s == 17) begin
73         s=0;
74         count=0;
75       end
76       else s++;
77     expectedResult = results[s];

```

Console

```

Design\project\project\src\wave.asdb
# 7:47 PM, Friday, January 27, 2023
# Simulation has been initialized
run
# KERNEL: fault free
# KERNEL: Simulation has finished. There are no more test vectors to simulate.
> asim -05 +access +w_nets +access +r +access +r+w traffic_light_TB

```

Figure 3

Deliberate error

```

58 module generate_test(input reg clk, reg go, reg rst, output reg [6:0] count=0, reg [7:0] expectedResult);
59 reg [6:0] state [0:17] = '{1,3,33,35,45,47,48,50,65,67,72,74,84,86,87,89,104,107};
60 reg [4:0] s = 0;
61 reg [7:0] results [0:17] = '{8'b10101000,8'b11111010,8'b00001010,8'b00011010,
62 8'b00101010,8'b01101010,8'b10101010,8'b10101111,8'b10100000,8'b10100001,
63 8'b10100010,8'b10100111,8'b10101000,8'b10101001,8'b10101010,8'b10111010,
64 8'b10001010,8'b10011010};
65 initial expectedResult = results[s];
66 always@(posedge clk) begin
67   if(rst) count=0;
68   else if(go) begin
69     count++;
70     if(count >= state[s])
71       if(s == 17) begin
72         s=0;
73         count=0;
74       end
75       else s++;
76     expectedResult = results[s];

```

Console

```

# 7:48 PM, Friday, January 27, 2023
# Simulation has been initialized
run
# KERNEL: faulty when counter = 0
# KERNEL: result = 10101010 <and> expectedResult = 10101000
# KERNEL: Simulation has finished. There are no more test vectors to simulate.
> asim -05 +access +w_nets +access +r +access +r+w traffic_light_TB

```

Figure 4

S0	10	10	10	10	1	0 and 107
----	----	----	----	----	---	-----------

```

58 module generate_test(input reg clk, reg go, reg rst, output reg [6:0] count=0, reg [7:0] expectedResult);
59 reg [6:0] state [0:17] = '{1,3,33,35,45,47,48,50,65,67,72,74,84,86,87,89,104,107};
60 reg [4:0] s = 0;
61 reg [7:0] results [0:17] = '{8'b10101010,8'b11111010,8'b11001010,8'b00011010,
62 8'b00101010,8'b01101010,8'b10101010,8'b10101111,8'b10100000,8'b10100001,
63 8'b10100010,8'b10100111,8'b10101000,8'b10101001,8'b10101010,8'b10111010,
64 8'b10001010,8'b10011010};
65 initial expectedResult = results[s];
66 always@(posedge clk) begin
67   if(rst) count=0;
68   else if(go) begin
69     count++;
70     if(count >= state[s])
71       if(s == 17) begin
72         s=0;
73         count=0;
74       end
75       else s++;
76   expectedResult = results[s];
77

```

Console

```

# 7:50 PM, Friday, January 27, 2023
# Simulation has been initialized
run
# KERNEL: faulty when counter = 3
# KERNEL: result = 00001010 <and> expectedResult = 11001010
# KERNEL: Simulation has finished. There are no more test vectors to simulate.
> asim -O5 +access +w_nets +access +r +access +r+w traffic_light_TB

```

Figure 5

S2	00	00	10	10	30	3
----	----	----	----	----	----	---

```

59 module generate_test(input reg clk, reg go, reg rst, output reg [6:0] count=0, reg [7:0] expectedResult);
60 reg [6:0] state [0:17] = '{1,3,33,35,45,47,48,50,65,67,72,74,84,86,87,89,104,107};
61 reg [4:0] s = 0;
62 reg [7:0] results [0:17] = '{8'b10101010,8'b11111010,8'b00011010,8'b00011010,
63 8'b00101010,8'b01101010,8'b10101010,8'b10101111,8'b10100000,8'b10100001,
64 8'b10100010,8'b10100111,8'b10101000,8'b10101001,8'b10101010,8'b10111010,
65 8'b10001010,8'b11111010};
66 initial expectedResult = results[s];
67 always@(posedge clk) begin
68   if(rst) count=0;
69   else if(go) begin
70     count++;
71     if(count >= state[s])
72       if(s == 17) begin
73         s=0;
74         count=0;
75       end
76       else s++;
77   expectedResult = results[s];
78

```

Console

```

# 7:52 PM, Friday, January 27, 2023
# Simulation has been initialized
run
# KERNEL: faulty when counter =104
# KERNEL: result = 10011010 <and> expectedResult = 11111010
# KERNEL: Simulation has finished. There are no more test vectors to simulate.
> asim -O5 +access +w_nets +access +r +access +r+w traffic_light_TB

```

Figure 6

S17	10	01	10	10	3	104
-----	----	----	----	----	---	-----

Conclusion and Future works

This system works with best effort way as possible but the test bench use the more confident way. Where the system use if statement side by side with increment to color code and test bench use memory. This to make the IC chip of the system needs less space so less cost and to make us surer with test bench results.

In future this system may be more scalable with time of color lights changes, for example may have two inputs works as multiplier factor number, one with highway streets open and farm streets close and other for farm streets open and highway streets close.